

## Pipelined FIR Filter with Parallelism ( $L = 3$ )

**1. Introduction and FIR Equation.** A finite impulse response (FIR) filter of length  $N = 211$  computes:

$$y[n] = \sum_{k=0}^{N-1} h_k x[n-k],$$


where  $h_k$  are signed 16-bit coefficients and  $x[n]$  are input samples. Our Verilog design uses:

- **Parallelism** ( $L = 3$ ) to process three MAC (multiply-accumulate) operations per iteration.
- **Pipelined stages** to improve throughput by breaking computation into smaller steps.

### 2. Design Structure.

- **Parameters:**  $N=211$ ,  $IN\_WIDTH=16$ ,  $COEF\_WIDTH=16$ ,  $MUL\_WIDTH=32$ , and  $ACC\_WIDTH=40$ .
- **Shift Register:** A 211-entry array (`shift_reg`) that holds recent input samples (new sample enters index 0).
- **Coefficient Array:** `COEFF[0:N-1]` stores the 211 FIR taps.
- **Chunks:** The 211 taps are grouped into  $\lceil 211/3 \rceil = 71$  chunks; each chunk handles 3 coefficient-sample multiplications.

 **3. Pipeline and FSM.** The filter uses six pipeline steps: sample latch, multiply, two add stages, accumulation, and final output. The FSM states:



- **ST\_MULT\_IN & ST\_MULT\_OUT:** Input registers drive three parallel multipliers, producing three 32-bit products.
- **ST\_ADD1 & ST\_ADD2:** Two add stages reduce partial products into a single sum.
- **ST\_ACC:** The partial sum is added to a 40-bit accumulator (`accum_reg`).
- **ST\_DONE:** Outputs the final filter result and asserts `data_out_valid`.

**4. Test Bench Summary.** A 100 MHz clock is generated, and an impulse (16'h4000) is fed as input to verify the impulse response. Once `data_out_valid` is high, the output is sampled for confirmation.

**5. Conclusion.** This parameterizable design efficiently handles large-tap FIR filters through  $L = 3$  parallelism. Multiple pipeline stages minimize the critical path by splitting multiply-and-accumulate operations. The accompanying test bench verifies correctness under impulse and zero-input scenarios.